

Total No. of Questions—12]

[Total No. of Printed Pages—4+2

Seat No.	
-------------	--

**[4857]-162****S.E. (E & TC/Electronics) (First Semester) EXAMINATION, 2015****SOLID STATE DEVICES AND CIRCUITS****(2008 PATTERN)****Time : Three Hours****Maximum Marks : 100****N.B. :-** (i) Answer *three* questions from each Section.

(ii) Answers to the two Sections should be written in separate answer-books.

(iii) Neat diagrams must be drawn wherever necessary.

(iv) Figures to the right indicate full marks.

(v) Use of electronic pocket calculator is allowed.

(vi) Assume suitable data, if necessary.

**SECTION I**

1. (a) For the diode shown in Fig. 1 calculate the currents  $I_1$  and  $I_2$  consider both the diodes having  $R_f = 10 \Omega$  and  $V_r = 0.6 \text{ V}$ . [6]

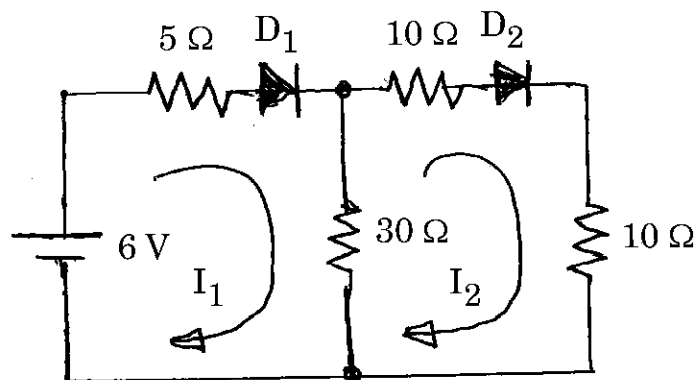


Fig. 1

P.T.O.

- (b) Write volt-ampere equation for a PN junction diode. Explain the significance of each symbol. Calculate the ideal current values in forward and reverse biased condition. [6]
- (c) Explain photodiode with respect to construction, working, characteristics and applications. [6]

*Or*

2. (a) Explain the following non-ideal current voltage characteristics of MOSFET : [9]
- (i) Finite output resistance
- (ii) Body effect
- (iii) Subthreshold conduction.
- (b) For the voltage divider bias circuit using EMOSFET has  $R_1 = 22 \text{ M}\Omega$ ,  $R_2 = 18 \text{ M}\Omega$ ,  $R_D = 3 \text{ k}\Omega$  and  $R_S = 820 \text{ }\Omega$ ,  $V_{DD} = 40 \text{ V}$ ,  $V_T = 5 \text{ V}$ ,  $I_{D(ON)} = 3 \text{ mA}$  at  $V_{GS(ON)} = 10 \text{ V}$ . Determine  $V_G$ ,  $R_G$ ,  $I_D$ ,  $V_{DS}$  and  $V_{GS}$ . [9]
3. (a) Draw and explain the following biasing techniques for EMOSFET. Also calculate  $V_{GS}$  and  $V_{DS}$  both techniques : [10]
- (i) Voltage divider bias
- (ii) Voltage feedback bias.
- (b) Determine  $A_V$ ,  $R_I$ ,  $R_o$  and  $r_o$  for the CS amplifier with voltage divider bias. This configuration has the following components  $R_1 = 22 \text{ M}\Omega$ ,  $R_2 = 18 \text{ M}\Omega$ ,  $R_D = 3 \text{ k}\Omega$  and  $R_S = 820 \text{ }\Omega$ ,  $V_{DD} = 40 \text{ V}$ ,  $V_T = 5 \text{ V}$ ,  $I_{D(ON)} = 3 \text{ mA}$  at  $V_{GS(ON)} = 10 \text{ V}$ ,  $\lambda = 0.03 \text{ V}^{-1}$ . [6]

*Or*

4. (a) Compare MOSFET with BJT. [4]  
 (b) Draw the high frequency model for MOSFET. [4]  
 (c) Explain the terms in brief : [8]  
     (i) BiCMOS technology  
     (ii) MOSFET Scaling.
5. (a) Derive the relation for  $A_i$ ,  $R_i$ ,  $A_v$ ,  $Y_o$ ,  $A_{vS}$  and  $A_{iS}$  for CE amplifier without  $R_E$ . [8]  
 (b) What is thermal runaway ? How to avoid it ? State the expression for power dissipation ( $P_D$ ) with significance. [8]

*Or*

6. (a) Compare Common Emitter, Common Base and Common Collector configurations of BJT. [4]  
 (b) Design the single stage BJT amplifier if  $V_{CC} = 12\text{ V}$ ,  $V_{CE} = 4.94\text{ V}$ ,  $I_C = 1.37\text{ mA}$ ,  $V_E = 0.63\text{ V}$ ,  $V_{BE} = 0.61\text{ V}$ ,  $S = 9$  and  $\beta = 300$ . [6]  
 (c) Write a short note on temperature compensation against  $V_{BE}$  and  $I_{CO}$  using diode. [6]

## SECTION II

7. (a) Define lower and upper cut-off frequencies of an amplifier. Why are these frequencies called as half power frequencies ? [6]

- (b) Write the formulae for  $A_V$  (low) and  $A_V$  (high) in terms of  $A_V$  (mid) and explain each term. [4]
- (c) An RC coupled amplifier has mid band gain  $A_V$  (mid) = 80 and the input resistance  $10\text{ k}\Omega$  is fed from an ideal source, through the coupling capacitor of  $0.22\text{ }\mu\text{F}$ . Calculate : [8]
- (i) The lower cut of frequency
- (ii) Voltage gain at 400 Hz
- (iii) The frequency at which gain is 10 dB down the mid band value.

*Or*

8. (a) Enlist the advantages of square wave testing method over frequency response method. [3]
- (b) In RC coupled amplifier derive the following relations : [7]
- $$t_r = 0.35 / f_H \text{ and } \% P = \pi f_L * 100 / f$$
- (c) Draw the high frequency  $\pi$  model of transistor and derive the expressions for  $g_m$ ,  $r_{bb'}$  and  $r_{b'e}$ . Write their typical values. [8]
9. (a) For the amplifier circuit shown in Fig. 2, identify the topology and find Gain, input impedance and output impedance with feedback. Assume  $h_{fe} = 50$  and  $h_{ie} = 1.1\text{ K}$ . [8]

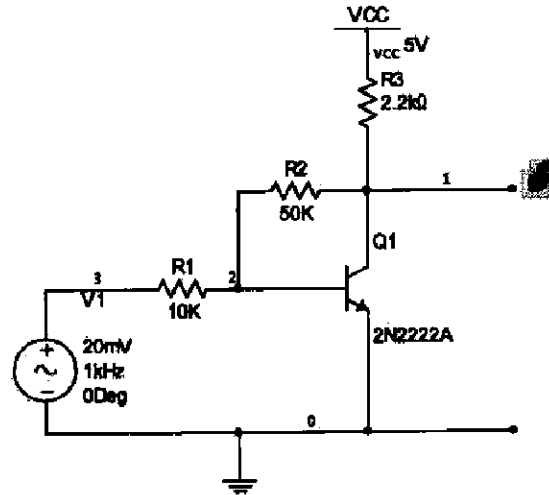


Fig. 2

- (b) Prove that the output impedance for voltage sampling decreases and input impedance for series mixing increases with negative feedback. [8]

*Or*

10. (a) State the Barkhausen criteria for sustained oscillations. Draw the circuit diagram of Colpitts' oscillator using BJT and derive the expression for frequency of oscillations. [8]
- (b) Compare Voltage series, Voltage shunt, current series and current shunt topology on the basis of Gain,  $R_o$ ,  $R_i$ , mixing and sampling. [8]
11. (a) Write a short note on three-point method of Harmonic distortion. [6]

- (b) How are the even harmonic distortions eliminated from class B push-pull amplifier ? [6]
- (c) Differentiate between class A, class B, and class AB Power Amplifier. [4]

*Or*

12. (a) For class B push-pull Amplifier supply voltage is +24 V. The amplifier is driving loudspeaker of resistance 8 ohms as load. If turns ratio of complete primary to secondary winding of output transformer is 4 : 1, calculate DC input power, AC output power, Efficiency and Power dissipation per transistor. [8]
- (b) Collector base junction of certain transistor dissipates 2 W of power. The thermal resistance from case to air is  $20^{\circ}\text{C}$  and junction to case is  $8^{\circ}\text{C}$  and free air temperature is  $25^{\circ}\text{C}$ . What is the junction temperature and case temperature ? [4]
- (c) Prove that the % efficiency for class A power amplifier is 25%. [4]