

Total No. of Questions—12]

[Total No. of Printed Pages—4

Seat No.	
-------------	--

[5057]-66

S.E. (Electronics/E&TC) (Second Semester) EXAMINATION, 2016
INTEGRATED CIRCUITS AND APPLICATIONS
(2008 PATTERN)

Time : Three Hours**Maximum Marks : 100**

- N.B. :-** (i) Answer *three* questions from Section I and *three* questions from Section II.
- (ii) Answers to the two Sections should be written in separate answer-books.
- (iii) Neat diagram must be drawn whenever necessary.
- (iv) Assume suitable data, if necessary.

SECTION I

1. (a) What is need of level shifter block in op-amp ? Explain different circuits used for level shifting. [10]
- (b) Explain how to improve CMRR of differential amplifier. Explain any *one* current source circuit. [8]
- Or*
2. (a) Derive the expression for differential gain, input resistance and output resistance for dual input balanced output differential amplifier using γ parameters. [10]
- (b) Draw the current mirror circuit with necessary derivation. [8]

P.T.O.

3. (a) What is need of frequency compensation ? State and explain the method of frequency compensation. [8]
- (b) State the reason of limiting the value of slew rate. Op-amp has slew rate of $2 \text{ V}/\mu\text{sec}$. Find the rise time of output voltage of 10 V amplitude resulting from a rectangular pulse input if the op-amp is slew rate limited. [8]

Or

4. (a) Explain the effect of temperature on : [8]
- (i) Input bias current
- (ii) Input offset current
- (iii) Input offset voltage
- (iv) Output offset voltage.
- (b) Write a note on low noise op-amp. [8]
5. (a) Explain the operation of summing differentiator. Derive its expression. [8]
- (b) Explain voltage to current converter with grounded load using op-amp. Mention its applications. [8]

Or

6. (a) Design a practical integrator circuit with a d.c. gain of 10, to integrate a square wave of 10 kHz. [8]
- (b) Draw the voltage follower using op-amp. Explain the working and its applications. [8]

SECTION II

7. (a) Explain various power supply performance parameters. [8]
(b) Write short notes on the following : [8]
(i) Clipper and clamper using op-amp
(ii) Instrumentation amplifier.

Or

8. (a) Draw the circuit of triangular wave generator and explain its operation. [8]
(b) Explain the working of inverting Schmitt trigger. [8]
9. (a) Explain working of any *two* ADC. Compare their performance. [8]
(b) Draw and explain the block diagram of IC 9400 for frequency to voltage conversion. [10]

Or

10. (a) Define the following terms for DAC : [8]
(i) Resolution
(ii) Accuracy
(iii) Conversion time
(iv) Monotonicity.
- (b) State the various methods of DA conversion. State advantages and disadvantages of each. [10]

11. (a) State the advantages of active filter. Also explain the operation of second order low pass filter. [8]
- (b) Design a second order band pass filter with $f_0 = 1$ kHz and bandwidth equal to 20 Hz. What is resonant gain ? [8]

Or

12. Write notes on (any *two*) : [16]
- (i) Active tone control
- (ii) PLL
- (iii) Audio amplifier using op-amp.

www.sppuonline.com