



[4658] – 83

Seat No.	
-------------	--

**T.E. (E&TC) (Semester – I) Examination, 2014
NETWORK SYNTHESIS AND FILTER DESIGN
(2008 Pattern)**

Time : 3 Hours

Max. Marks : 100

- Instructions :** 1) Answer Q. 1 or Q. 2, Q. 3 or Q. 4, Q. 5 or Q. 6 from Section I and Q. 7 or Q. 8, Q. 9 or Q. 10, Q. 11 or Q. 12 from Section II.
2) Answers to the **two** Sections should be written in **separate** books.
3) **Neat** diagrams must be drawn **wherever** necessary.
4) Assume **suitable** data if **necessary**.

SECTION – I

1. a) Define Network synthesis. State the properties of Network functions. 4
b) Test whether the following polynomial is Hurwitz 6
 $F(s) = s^4 + s^3 + 5s^2 + 3s + 4$
c) Synthesize the following p.r. impedance function using elementary synthesis procedure. 8

$$Z(s) = \frac{6s^3 + 3s^2 + 3s + 1}{6s^3 + 3s}$$

OR

2. a) Check whether the following are stable network functions. 4
i) $\frac{s}{s^2 - 3s + 4}$
ii) $\frac{s-1}{s^2 + 4}$
b) Which of the following are p.r.f. functions ? Give reasons. 6
i) $\frac{s+2}{s^2 + 3s + 2}$
ii) $\frac{3s^2 + 5}{s(s^2 + 1)}$
c) Synthesize the following impedances by successive removals of $j\omega$ axis poles or by removing $\min[\text{Re}(j\omega)]$. 8
i) $\frac{s^3 + 4s}{s^2 + 2}$
ii) $\frac{s+1}{s(s+2)}$

P.T.O.

[4658] – 83

-2-



3. a) Indicate which of the following functions are either R-C, R-L, or L-C impedance functions. **6**

i) $Z(s) = \frac{s^3 + 2s}{s^4 + 4s^2 + 3}$

ii) $Z(s) = \frac{s^2 + 6s + 8}{s^2 + 4s + 3}$

iii) $Z(s) = \frac{s^2 + 4s + 3}{s^2 + 6s + 8}$

- b) Synthesize the following function by continued fractions expansion method. **4**

$$Z(s) = \frac{s^2 + 2s + 2}{s^2 + s + 1}$$

- c) Synthesize the following function by Partial Fraction expansion method. **6**

$$Z(s) = \frac{3(s+2)(s+4)}{s(s+3)}$$

OR

4. a) State the properties of R-C driving-point impedances and R-L driving-point impedances. **6**

- b) Synthesize the following function by continued fraction expansion method. **4**

$$Z(s) = \frac{(s^2 + 1)(s^2 + 3)}{s(s^2 + 2)}$$

- c) Synthesize the following function by partial fraction expansion method. **6**


$$Z(s) = \frac{2(s+1)(s+3)}{(s+2)(s+6)}$$

5. a) State the properties of Transfer functions. **4**

- b) Synthesize the following function with 1-Ω termination. **6**

$$Z_{21}(s) = \frac{2}{s^3 + 3s^2 + 4s + 2}$$

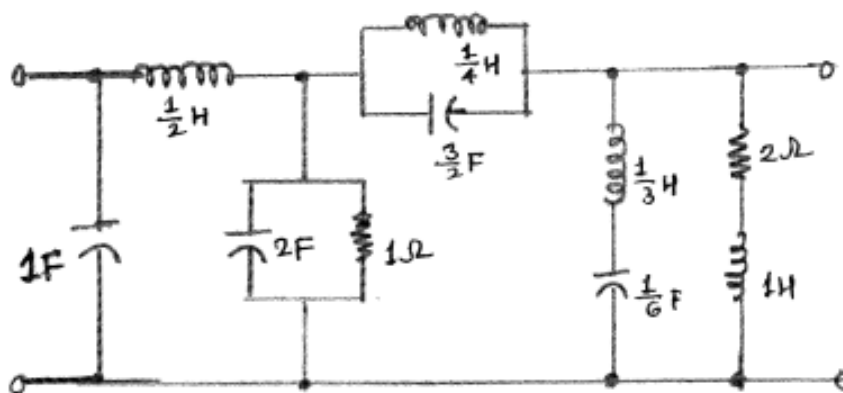- c) Identify the zeros of transmission for the given network. **6**



OR



6. a) Synthesize the following voltage ratio with $1-\Omega$ termination using Lattice network. 4

$$\frac{V_2}{V_1} = \frac{1}{2} \cdot \left(\frac{s-1}{s+1} \right)$$

- b) Synthesize the following function with $1-\Omega$ termination. 6

$$Z_{21}(s) = \frac{s^3}{s^3 + 3s^2 + 4s + 2}$$

- c) Synthesize the following voltage ratio with $1-\Omega$ termination using Bridge – T network. 6

$$\frac{V_2}{V_1} = \frac{s^2 + 1}{s^2 + 2s + 1}$$

SECTION – II

7. a) State the characteristics of Butterworth and Chebyshev approximations. 4

- b) Derive the expression for transfer function of normalized low-pass filter of second-order butterworth filter. 6

- c) Synthesize third-order low-pass Butterworth passive filter for the following specifications :
 $R_0 = 500\Omega$ and $\omega_c = 10^4$ rad/sec. 8

OR

8. a) Explain frequency scaling and impedance scaling. 6

- b) Transform the third-order Butterworth normalized low-pass passive filter into a high-pass filter with 500Ω impedance level with cut-off frequency $\omega_0 = 10^6$ rad/sec. 8

- c) Write a short note on Chebyshev approximations. 4

9. a) Draw a neat diagram of positive feedback topology. And derive the transfer function of the positive feedback topology assuming an ideal op-amp. 10

- b) Write a short note on RC-CR transformation. 6

OR

10. Synthesize a second-order Bandpass filter with a centre frequency of 1000 rad/sec and a pole Q of 10. The gain at the centre frequency is required to be 0 dB. 16

[4658] – 83

-4-



11. a) Define sensitivity. And derive an expression for the sensitivity of ω_p and K (DC gain constant) to the component values R_1 , R_2 , C_1 , C_2 , r_1 and r_2 for given transfer function of lowpass sullen and key circuit for $n = 2$ (order of filter). 8

$$T(s) = \frac{K / R_1 R_2 C_1 C_2}{s^2 + s \left(\frac{1}{R_1 C_1} + \frac{1}{R_2 C_1} + \frac{1-K}{R_2 C_2} \right) + \frac{1}{R_1 R_2 C_1 C_2}}$$

- b) Write a short note on op-amp frequency characteristics and compensation techniques. 8

OR

12. Write a short note on following : 16

- i) FDNR
- ii) Gyrator
- iii) NIC
- iv) Multielement deviation.

B/II/14/

 www.sppuonline.com